

# Computer Organisation & Architecture

positive logic and negative logic:

→ positive logic:

Here, we denote high voltage is 1 & low voltage is represented as 0.

eg →

A	B	$y = A \text{ op } B$
L	L	L
L	H	L
H	L	L
H	H	H

→

A	B	y
0	0	0
0	1	0
1	0	0
1	1	1

↓  
AND op.

High	→ 1
Low	→ 0

→ Negative logic:

High	→ 0
Low	→ 1

A	B	$y = A \text{ op } B$
1	1	1
1	0	1
0	1	1
0	0	0

→ OR op.

the logic  $\rightarrow$  AND opr.  
+ -ve logic  $\rightarrow$  OR opr.

we ~~are~~ <sup>always</sup> use the logic for developing digital circuit.

$\rightarrow$  Basic logic gates :

- 1) OR ( $A+B$ )
- 2) AND ( $A \cdot B$ )
- 3) NOT ( $\bar{A}$ )


1) OR gate.

A	B	$Y = A+B$
0	0	0
0	1	1
1	0	1
1	1	1



2) AND gate.

A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

 


3) NOT gate.


A	$Y = \bar{A}$
0	1
1	0



 - 2
- 1)  $F = \bar{A}\bar{B} + CD + \bar{E}F$
  - A) 6 inputs  $\rightarrow A, B, C, D, E, F$



2)  $F = (\bar{A}+B)(A+C)(B+C)$

 




# \* Universal Gates :

## 1) NAND :

\* Combination of AND gate NOT gate

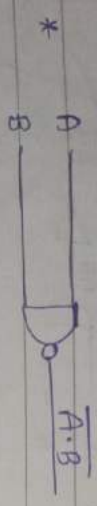

A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0


AND-gate and complement  
 $Y = \overline{A \cdot B}$

NOT gate has only 1 input

→ Universal Gates properties : (NAND).

① \* NOT gate implementation with NAND gate


\* NOT → 1 input  
NAND → 2 input

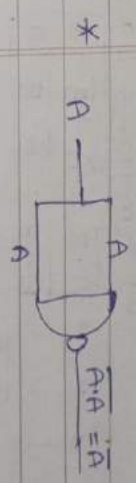

$A \cdot A = \bar{A}$   
 $\therefore A \cdot A = \bar{A}$

② \* AND gate implementation with NAND gate:


\* AND → 2 input  
NAND → 2 input

 

$\bar{A} \cdot \bar{A} = \bar{A}$   
 $\bar{A} \cdot B \cdot \bar{A} \cdot B = \bar{A} \cdot B$   
 $\therefore \bar{A} \cdot B = \underline{A \cdot B}$

## 2) NOR :

\* Combination of OR and NOT gate

 


A	B	$Y = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

OR-gate and complement  
 $Y = \overline{A + B}$

③ \* OR gate implementation with NAND gate:  
OR → 2 inputs  
NAND → 2 inputs

(vi)  $\rightarrow$  gate.

 

①

$$\bar{A} \cdot \bar{B} = \overline{A+B}$$

by DeMorgan's Law,

$$\bar{A} \cdot \bar{B} \rightarrow \overline{A+B} = \bar{A} + \bar{B}$$


$$\bar{A} + \bar{B} = \overline{A \cdot B}$$

$\rightarrow$  Universal gate properties (NOR):

① NOT gate implementation with NOR gate




② AND gate implementation with NOR (vi).

 

$$\bar{A} + \bar{B} = \overline{A \cdot B} = \bar{A} \cdot \bar{B} = A \cdot B$$

(by DeMorgan's)

 ③ ~~NOR~~ OR (vi) implementation with NOR (vi):



$$\overline{A+B} + \overline{A+B} = \overline{A+B} \cdot \overline{A+B} = \overline{A+B} = A+B$$

(DeMorgan's)

$\rightarrow$  Exclusive OR  $\rightarrow$  XOR  $\rightarrow$  '⊕' symbol  
Exclusive NOR  $\rightarrow$  XNOR  $\rightarrow$  '⊙' symbol

\* XOR:

\* It produces 1st = 1 when odd no. of inputs are 1.





\*  $Y = A \oplus B$

A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

odd  $\rightarrow$   
 $0+1=1$   
 $1 \rightarrow \text{odd} \rightarrow 1$

\* SOP (Sum of product)  $\rightarrow$  based on truth table.

$Y = A \oplus B$  from column  $\rightarrow$  1 in column

Example  $\rightarrow$  then 0  $\rightarrow$  complement

Example  $\rightarrow$  1 for 5 row.

eg  $\rightarrow Y = \bar{A}B + A\bar{B}$  (above T-table).

\* POS (product of sum)  $\rightarrow$  based on truth table.

Example

$Y = A \oplus B$  from column  $\rightarrow$  0 in column

Example  $\rightarrow$  then 1  $\rightarrow$  complement

eg  $\rightarrow Y = (A+B)(\bar{A}+\bar{B})$  (above T-table)


\* XNOR:

\* produces 1 when even no of inputs are 1.

\*  $Y = A \odot B$

A	B	$Y = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

$0+0=1$   
 $0+1=0$   
 $1+1=1$

 


\* SOP  $Y = \bar{A}\bar{B} + AB$  (consider 1)  
POS  $Y = (A+B)(\bar{A}+\bar{B})$  (consider 0)

$\rightarrow$  combinational logic circuit:

\* It consists of input variables, logic gate & output variables

\* logical gate accept signals from inputs & generate signals to the outputs.

\* A block diagram of a logic circuit:

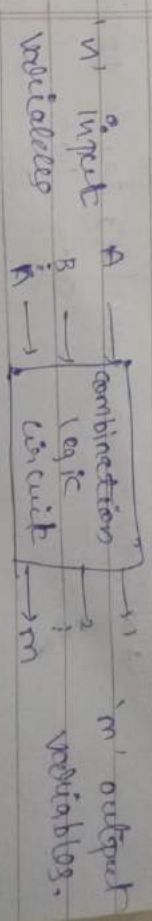

\* In C-logic circuit depending on the input, it produces same output.

\* There is no memory element to store previous element's output.

\* Step to develop C.L circuit:

- The problem is stated.
- The no. of available input variables & required output variables is determined.
- The input & output variables are assigned letter symbols.
- The truth table that defines the required relationship b/w input & output is derived.
- The simplified boolean C's for each output is obtained.
- The logic diagram is drawn.

1) Adder: (for adding purpose)

→ Half Adder → 2 inputs, 2 outputs


$$\begin{array}{r} 10 \\ 10 \\ \hline 20 \end{array}$$

→ Full Adder → 3 inputs, 2 outputs

$$\begin{array}{r} 10 \\ 10 \\ 10 \\ \hline 30 \end{array}$$

1) Half Adder:

\* 2 inputs & 2 outputs

 


A	B	S	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{SOP } S = \bar{A}B + A\bar{B} = A \oplus B$$

$$\text{SOP } \text{Cout} = AB$$

\* Half adder circuit:

 


2) Full Adder:

\* used for addition

\* 3 inputs & 2 outputs



 

A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$S = 0 \rightarrow 01010$


$1+1 = 01$

$1+1+0 = 01+1 = 11$

$$SOP\ S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$

$$SOP\ C_{out} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

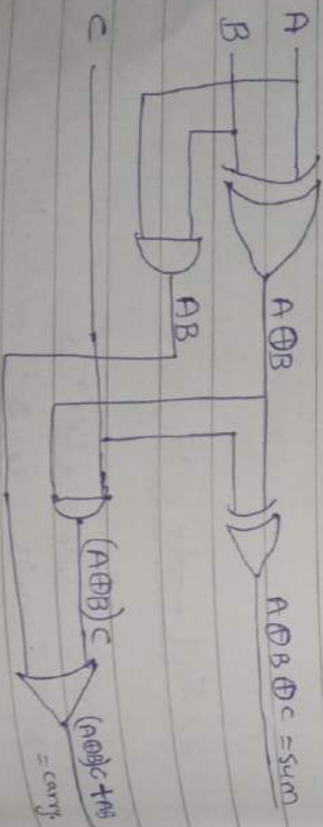To draw full Adder  $\rightarrow$  2 half adders & 1 OR gate



$\rightarrow$  Binary parallel Adder (Ripple carry adder):



For 4 Full Adders we need 4 Full Adders.


When we want to add 1011 & 0011 then we can't add with only 1 Full adder. So, here we are using series of Full adder.

There is 'n' bits, then 'n' no. of full adder needed.

C <sub>in</sub>	1	1	0	0	1	1	0	0	1	1
A	1	0	1	1	1	1	1	1	1	1
B	0	0	1	1	1	1	1	1	1	1
S	1	1	1	1	0	1	1	1	1	1
C <sub>out</sub>	0	0	1	1	1	1	1	1	1	1

LSB  $\rightarrow$  10

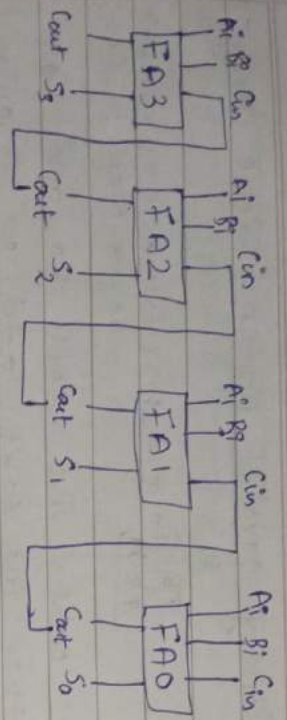Here, last significant bit always 0 (carry) there is no addition before. The carry (C<sub>out</sub>) will move to C<sub>in</sub> after each bit addition. Here, we are using 4 full adders bcz it has 4 bits.



Sum (S) = 01110  
Carry (Cout) = 0011

~~Cout not needed  
Cin = 0 (no carry in)  
no propagation delay  
at output~~

In this circuit FA1 will be worked only after getting the 1st Cout from FA0 & so on, so there is a delay for this propagation.  
The delay is from left to right. ( $\leftarrow$ )  
This propagation is  $\rightarrow$  carry propagation delay, so that's why it is also  $\rightarrow$  ripple carry adder.

$\rightarrow$  Decoder:


- \* It is combinational logic circuit.
- \* The basic C of decoders is detects a presence of some input combinations & indicates specific

- \* Output level.
- \* If there is a  $n$  input combination then max  $m \leq 2^n$  output combination.
- \* eg  $\rightarrow 2 \times 4, 3 \times 8, 4 \times 16$   
(2 input - 4 output)

a) Basic Binary Decoder:

eg  $\rightarrow$  ~~1001~~ 1001 combination assigned 2 outputs  
[1 0 1 0, even no. of 1s assigned  $\rightarrow$  0 produce]


logical circuit:

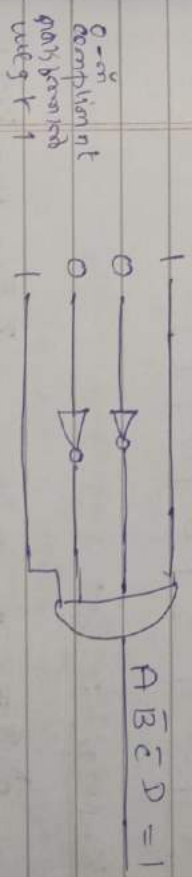

~~here we are using AND gate~~  
for eg, take the combination 1001 = 1  
and for all other combination it produces 0.  
In this eg we are using AND gate (all produces 0)  
(egs input - 1, 0 and 0 and 1 AND gate used)



2x4 line decoder:  
\* 2 inputs & 4 o/p

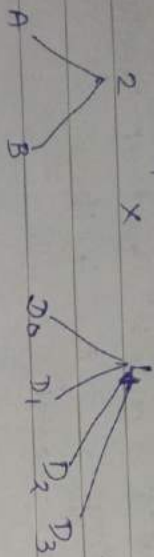

\* Truth table:

A	B	$D_0$	$D_1$	$D_2$	$D_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

using K-map:

A \ B	$\bar{B}$	B
$\bar{A}$	$\bar{A}\bar{B} D_0$	$\bar{A}B D_1$
A	$AB D_2$	$AB D_3$

$$D_0 = \bar{A}\bar{B}$$


$$D_1 = \bar{A}B$$

$$D_2 = AB$$


$$D_3 = AB$$

$$\begin{aligned}\bar{A}\bar{B} &\rightarrow 0 \text{ to } 1 \\ \bar{A}B &\rightarrow 1 \\ AB &\rightarrow 1 \\ AB &\rightarrow 1\end{aligned}$$

\* Logical circuit:

 

 Here we are ~~using~~ designing decoder logic circuit using AND gate. So it is in active high. Suppose we are designing with NAND gate, then it is active low.  
\* AND gate implementation:  
(active high)




\* NAND gate Implementation:  
(active low)




\* AND logic symbol:



\* NAND logic symbol:

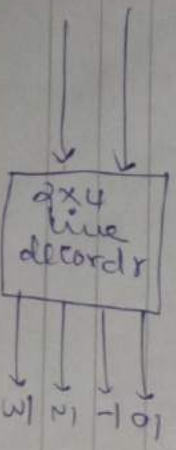

c) 3x8 line decoder:

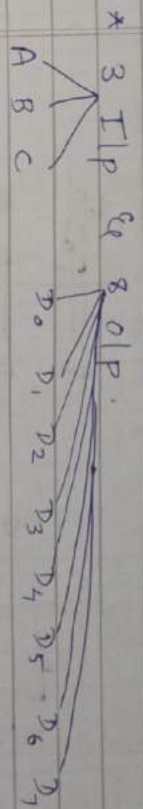

\* Truth Table:

A	B	C	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

A	B	C	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Key

eg →

$$D_0 = \bar{A} \bar{B} \bar{C}$$

$$D_1 = \bar{A} \bar{B} C$$

$$D_2 = \bar{A} B \bar{C}$$

$$D_3 = \bar{A} B C$$

$$D_4 = A \bar{B} \bar{C}$$


$$D_5 = A \bar{B} C$$

$$D_6 = A B \bar{C}$$


$$D_7 = A B C$$



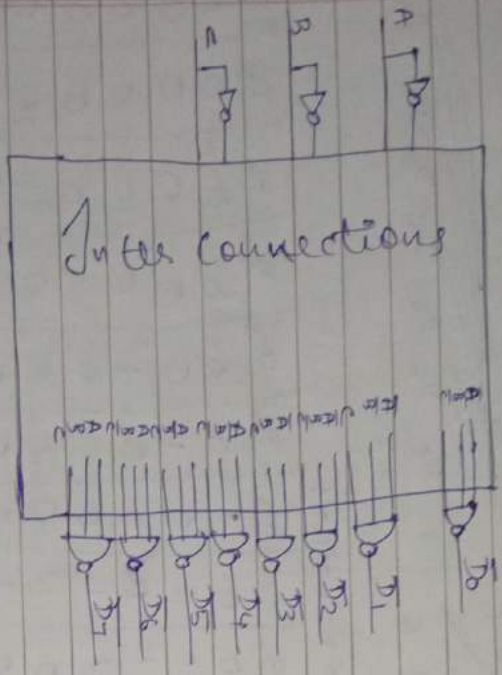
Here we are implementing Active low 3x8 Decoder using NAND gate



\* Logic Symbol:

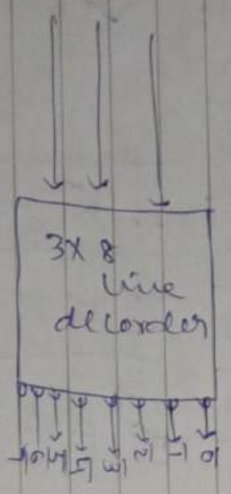

d) 4x16 line decoder:

 

A	B	C	D	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	D <sub>8</sub>	D <sub>9</sub>	D <sub>10</sub>	D <sub>11</sub>	D <sub>12</sub>	D <sub>13</sub>	D <sub>14</sub>	D <sub>15</sub>
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1

eg →

$$D_0 = \overline{A}\overline{B}\overline{C}\overline{D}$$

$$D_1 = \overline{A}\overline{B}\overline{C}D$$

$$D_2 = \overline{A}\overline{B}C\overline{D}$$

$$D_3 = \overline{A}\overline{B}CD$$

$$D_4 = \overline{A}B\overline{C}\overline{D}$$

$$D_5 = \overline{A}B\overline{C}D$$

$$D_6 = \overline{A}B C\overline{D}$$

$$D_7 = \overline{A}B C D$$

$$D_8 = A\overline{B}\overline{C}\overline{D}$$

$$D_9 = A\overline{B}\overline{C}D$$

$$D_{10} = A\overline{B} C\overline{D}$$


$$D_{11} = A\overline{B} C D$$

$$D_{12} = A B\overline{C}\overline{D}$$


$$D_{13} = A B\overline{C}D$$

$$D_{14} = A B C\overline{D}$$

$$D_{15} = A B C D$$

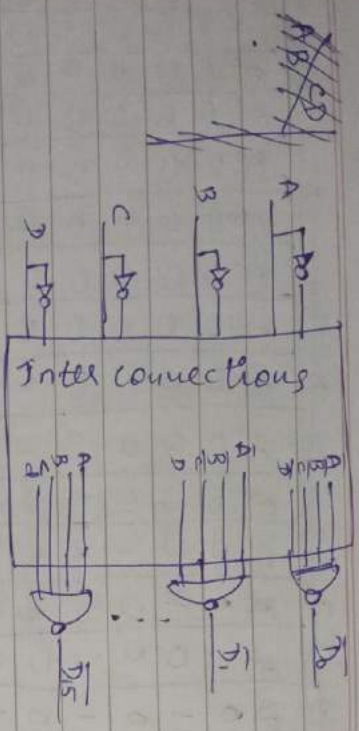


\* Logic circuit:

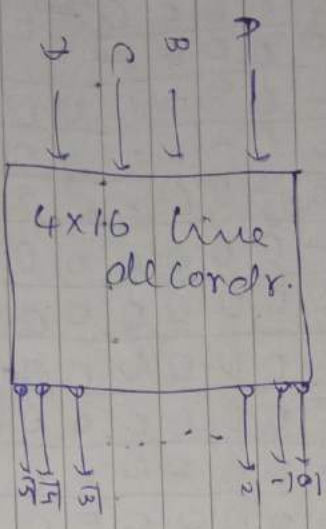

→ BCD to 7 segment decoder:

 B<sub>10</sub>D → 0-9 (decimal)  
eg → calculator (0-9)  
In cal, 8 is displayed as



\* When a decimal no. is representing in a digital screen it needs 7

Segments / 7 LED's.

\* Here we are using the input as BCD & we get a particular output

(def) \* It is combinational logic circuit which has input binary code usually BCD & convert the input into 7 segment output LED's.

Decimal no = 0 to 9.

$\begin{matrix} a \\ f \\ b \\ c \\ d \\ e \\ g \end{matrix}$  (this order is imp)

Here, each 1 is a LED (a, b, c, d, e, f, g) So there are 7 LED's. So that's it is → 7 segment decoders.

0	1	2	3	4	5	6	7	8	9
$\begin{matrix} a \\ f \\ b \\ c \\ d \\ e \\ g \end{matrix}$	$\begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \end{matrix}$	$\begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \end{matrix}$	$\begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \end{matrix}$	$\begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \end{matrix}$	$\begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \end{matrix}$	$\begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \end{matrix}$	$\begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \end{matrix}$	$\begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \end{matrix}$	$\begin{matrix} a \\ b \\ c \\ d \\ e \\ f \\ g \end{matrix}$

No. of inputs = 9

BCD code upto 9 will be the output. The relation ship b/w I/P & O/P:



Decimal	8	4	2	1	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	0	0	1
3	0	0	1	1	1	1	1	0	0	1	1
4	0	1	0	0	1	1	0	0	1	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	0	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	1	1	1

\* look on-wise  $a \rightarrow \sum m(0, 2, 3, 5, 6, 7, 8, 9)$

(a-norm (el-conv) 1 2 3 4 5 6 7 8 9) avoid 0 and 9 (no-999)

- \*  $b = \sum m(0, 1, 2, 3, 4, 7, 8, 9)$
- \*  $c = \sum m(0, 1, 3, 4, 5, 6, 7, 8, 9)$
- \*  $d = \sum m(0, 2, 3, 5, 6, 8, 9)$
- \*  $e = \sum m(0, 2, 6, 8)$
- \*  $f = \sum m(0, 4, 5, 6, 8, 9)$
- \*  $g = \sum m(2, 3, 4, 5, 6, 8, 9)$



a to g Again 2, 3, 4, 5, 6, 7, 8, 9 are take e only. for drawing logical circuit

DE  $\rightarrow 2^N \rightarrow 2^N$   
EN  $\rightarrow 2^N \rightarrow 2^N$

$e = \sum m(0, 2, 6, 8)$

0  $\rightarrow \bar{a}\bar{b}\bar{c}\bar{d}$   
2  $\rightarrow \bar{a}\bar{b}c\bar{d}$   
6  $\rightarrow \bar{a}b\bar{c}\bar{d}$   
8  $\rightarrow a\bar{b}\bar{c}\bar{d}$

  $e \rightarrow \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}b\bar{c}\bar{d} + a\bar{b}\bar{c}\bar{d}$



$\rightarrow$  Encoders:

DE  $\rightarrow$  2x4  
EN  $\rightarrow$  4x2

classmate  
Date \_\_\_\_\_  
Page \_\_\_\_\_


I 4 to 2 Encoder:  
4 I/P & 2 o/p.  
4  $\rightarrow$  D<sub>0</sub>, D<sub>1</sub>, D<sub>2</sub>, D<sub>3</sub>  
2  $\rightarrow$  A, B.

\* Truth table:

D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	A	B
0	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

eg  $\rightarrow$  A  $\rightarrow$  D<sub>2</sub> + D<sub>3</sub>  
B  $\rightarrow$  D<sub>1</sub> + D<sub>3</sub>

(check like this)

 


II 8 to 3 Encoder:

8  $\rightarrow$  D<sub>0</sub> - D<sub>7</sub>  
3  $\rightarrow$  A, B, C

D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	A	B	C
0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 eg  $\rightarrow$  A  $\rightarrow$  D<sub>4</sub> + D<sub>5</sub> + D<sub>6</sub> + D<sub>7</sub>  
B  $\rightarrow$  D<sub>2</sub> + D<sub>3</sub> + D<sub>6</sub> + D<sub>7</sub>  
C  $\rightarrow$  D<sub>1</sub> + D<sub>3</sub> + D<sub>5</sub> + D<sub>7</sub>




A, B, C  $\rightarrow$  3 rows  
Date \_\_\_\_\_  
Page \_\_\_\_\_



⇒ Multiplexers & De-multiplexers :

→ Multiplexers (MUX) :

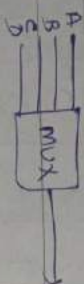

$n \rightarrow 1$  [  $n$  no. of I/p  $\rightarrow$  1 o/p ]  
we get only 1 o/p

[  $n$  ' input pass independently  
no. of I/p systems & output  
Select  $n$  mux-m &  
we get certain o/p. ]

\* MUX is a device that allows digital

signals from several sources to be

routed onto a single line of o/p.

\* Has several I/p lines & single o/p line.

\* Has also data selector lines which

specifies which I/p ~~the~~ signal has to

be switched to the o/p line.

\* 'n' data selector lines are required

for routing  $2^n$  I/p lines.


• 2 I/p lines  $\rightarrow$  1 selection line ( $2^0 = 2$ )

• 4 " "  $\rightarrow$  2 " ( $2^2 = 4$ )

• 8 " "  $\rightarrow$  3 " ( $2^3 = 8$ )


• 16 " "  $\rightarrow$  4 " ( $2^4 = 16$ )


\* n to 1 MUX Block diagram :

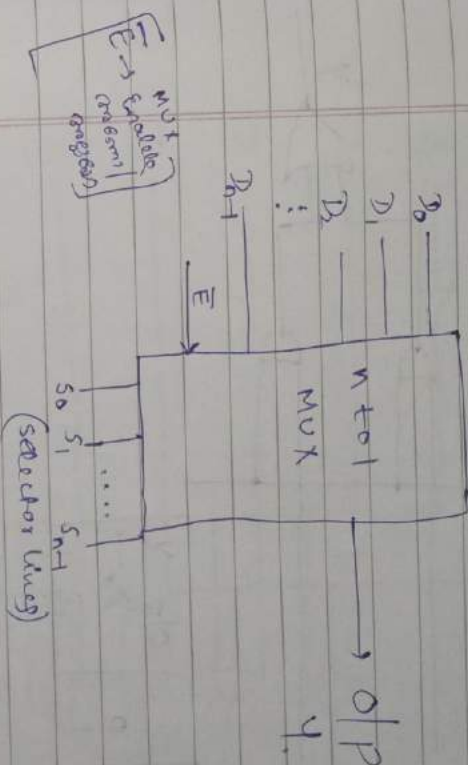

 1. 2 to 1 MUX :

\* 2 I/p data line and 1 o/p line. &  
1 selection line ( $2^0$ )  
Block diagram :



 



S	0	1
0	D <sub>0</sub>	D <sub>1</sub>
1	D <sub>1</sub>	D <sub>0</sub>

$\therefore Y = D_0 S' + D_1 S$

## II. 4 to 1 MUX :

\* A 4 to 1 MUX has 2 data selector lines ( $2^2=4$ ), a combination of which are used to select any of the 4 data IP lines.

\* Block diagram:

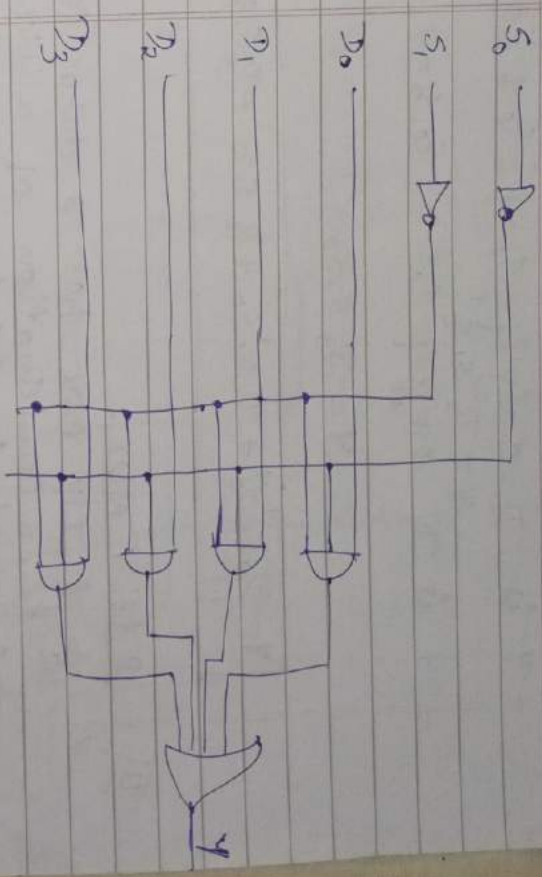 

S <sub>1</sub>	S <sub>0</sub>	Y
0	0	D <sub>0</sub>
0	1	D <sub>1</sub>
1	0	D <sub>2</sub>
1	1	D <sub>3</sub>

- Y is D<sub>0</sub> only if S<sub>1</sub>=0 & S<sub>0</sub>=0.

$\therefore Y = D_0 S_1' S_0'$

- Y is D<sub>1</sub> only if S<sub>1</sub>=0 & S<sub>0</sub>=1

$Y = D_1 S_1' S_0$



-  $y$  is  $D_2$  only if  $s_1 = 1$  &  $s_0 = 0$ .

$$y = D_2 s_1 s_0'$$

-  $y$  is  $D_3$  only if  $s_1 = 1$  &  $s_0 = 1$



$$\therefore y = D_3 s_1 s_0$$

$$y = D_0 s_1' s_0' + D_1 s_1' s_0 + D_2 s_1 s_0' + D_3 s_1 s_0$$

### III 8 to 1 MUX:

\* A 8 1P MUX has 3 data selector ( $2^3 = 8$ ), a combination of which are used to select any of 8 data lines

\* Block diagram:

  

$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$D_0$
0	0	1	$D_1$
0	1	0	$D_2$
0	1	1	$D_3$
1	0	0	$D_4$
1	0	1	$D_5$
1	1	0	$D_6$
1	1	1	$D_7$

$$\begin{aligned}
 Y &= D_0 S_2' S_1' S_0' \\
 Y &= D_1 S_2' S_1' S_0 \\
 Y &= D_2 S_2' S_1 S_0' \\
 Y &= D_3 S_2' S_1 S_0 \\
 Y &= D_4 S_2 S_1' S_0' \\
 Y &= D_5 S_2 S_1' S_0 \\
 Y &= D_6 S_2 S_1 S_0' \\
 Y &= D_7 S_2 S_1 S_0
 \end{aligned}$$


$$Y = D_0 S_2' S_1' S_0' + D_1 S_2' S_1' S_0 + \dots + D_7 S_2 S_1 S_0$$

→ MUX tree:

~~Diagram~~

- \* Bigger mux obtained by combining smaller mux.
- \* MUX with more no. of I/p can be

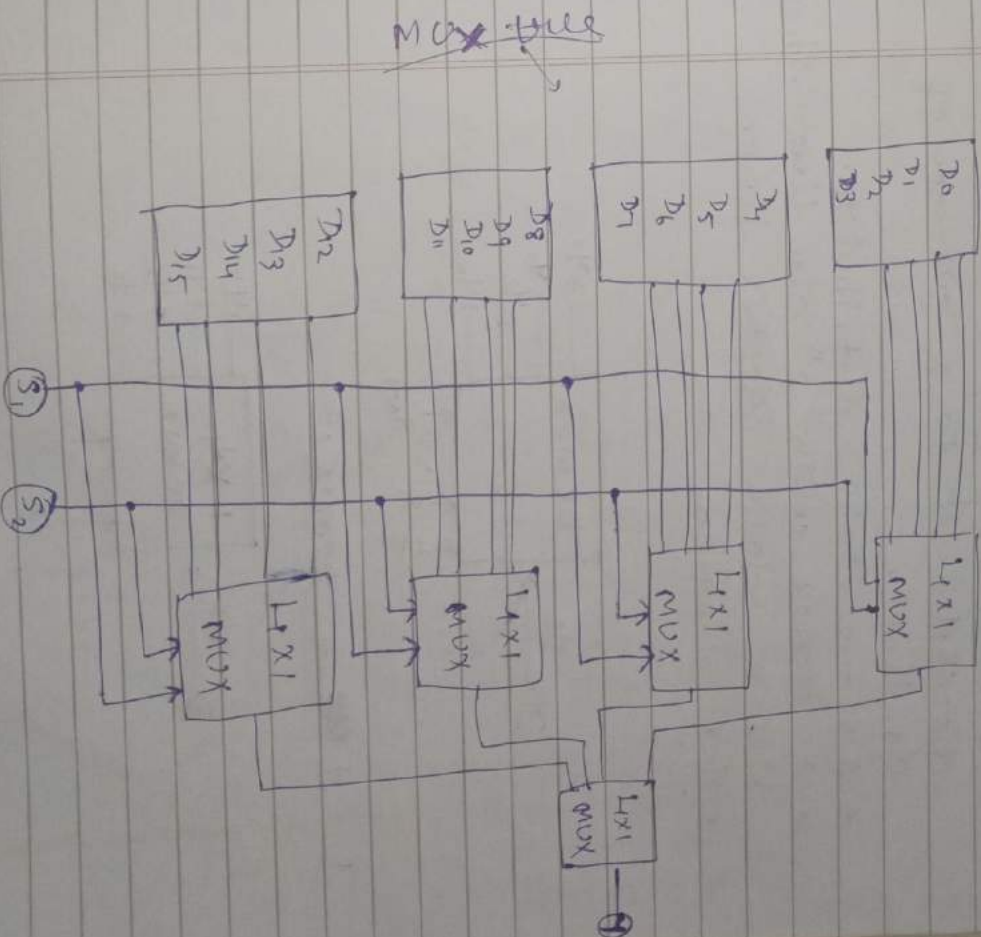
obtained cascading 2 or more mux with less no. of I/p.  
eg → for 16x1 mux, we need 4 mux.





 
## → DEMUX:

- \* 1 I/p line & 'n' no. of o/p.
- \* A DEMUX performs the reverse of a MUX.
- \* It takes I/p from 1 line & distributes it to a given no. of o/p lines.
- \* Also → Data distributor.
- \* A DEMUX with 2<sup>n</sup> o/p line should have 'n' data selector line.
- \* Block diagram →



## I 1 X 4 DEMUX:

 

\*

A 1 to 4 DEMUX has a single I/p (D), 2 selection lines ( $s_1, s_0$ ) & 4 o/p lines ( $y_0, y_1, y_2, y_3$ )

\* The I/p data goes to any 1 of the 4 o/p at a given time for a particular combination of select line.

\* Truth table →

Data	Select	Outputs					
Input (D)	Input						
	$s_1$	$s_0$	$y_3$	$y_2$	$y_1$	$y_0$	
D	0	0	0	0	0	D	
D	0	1	0	0	D	0	
D	1	0	0	D	0	0	
D	1	1	D	0	0	0	

egs →

$$\begin{aligned}
 y_0 &= \bar{s}_1 \bar{s}_0 \\
 y_1 &= \bar{s}_1 s_0 \\
 y_2 &= s_1 \bar{s}_0 \\
 y_3 &= s_1 s_0
 \end{aligned}$$

$S_1$     $S_0$     $D$  (input signal)

